

INEL 4207 Take Home Test

Use the following Specs if they are not stated in the problem.

$$V_{DD}=6\text{ V} \quad u_n C_{ox}=4 \cdot 229 \text{ uA/V}^2 \quad V_{TN0}=0.59\text{ V} \quad V_{TP0}=0.77\text{ V} \quad (W/L)_N=44 \quad (W/L)_P=4$$

$$C_L=80\text{ pF} \quad \gamma=0.016\sqrt{V} \quad 2\phi F=0.6\text{ V} \quad \beta=28 \quad V_{BE}=0.7\text{ V}$$

Answer each question thoroughly. Show your equations and justify your assumptions. Write all your answers on the answer sheet and submit it with all calculations. Make sure all units are clearly stated.

1. Using figure 1 connect a Capacitor C_L on its output and determine the following:
 - a. What digital function implemented?
 - b. Calculate V_{OH} and V_{OL} taking into account the body effect.
 - c. Calculate t_r , (t rise)

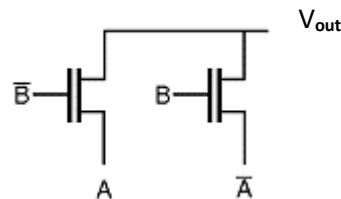


Fig. 1

2. Design a domino A+B+C with a PMOS equivalent transistor of 4 and an equivalent NMOS Transistor =44
 - a. Draw the net or graph (grafo) representing the Pull Down network of your circuit
 - b. Calculate the W/L of equivalent NMOS and PMOS transistor
 - c. Calculate V_{OH} and V_{OL} of the previous circuit and t_{phl} (propagation from high to low)
3. Read carefully and use **Figure 2** to answer
 - a. Determine V_{ref} (V_R) if $V_{BE}=V_{D1}=V_{D2}=0.75\text{ V}$ for $I=1\text{ mA}$ and $\beta=28$ for all BJT.

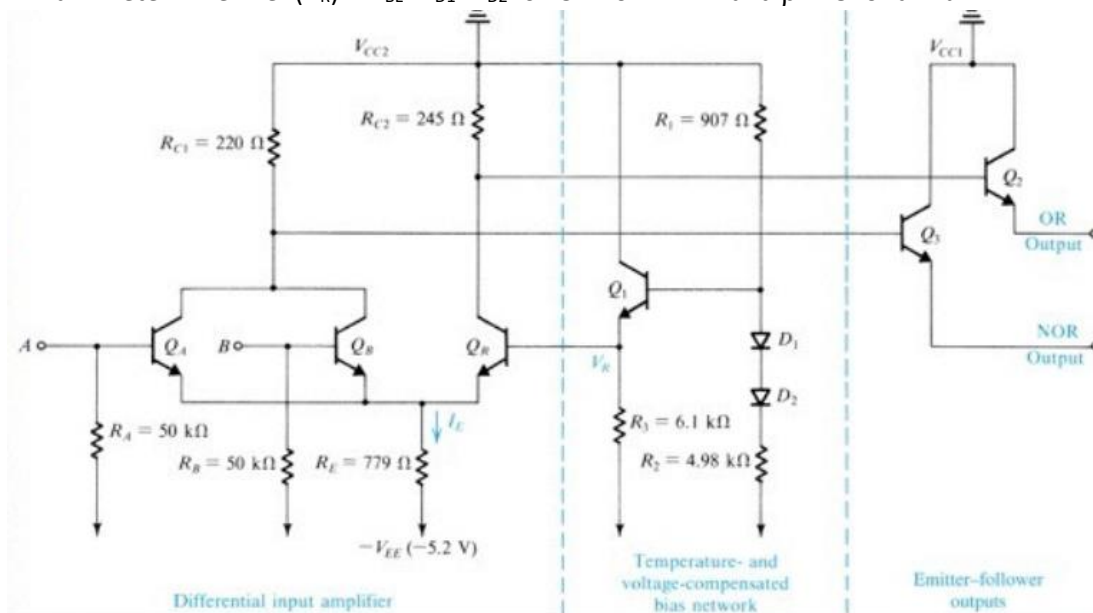


Fig. 2 ECL circuit

4. Answer using the following figure 3 (a), (b) and (c)

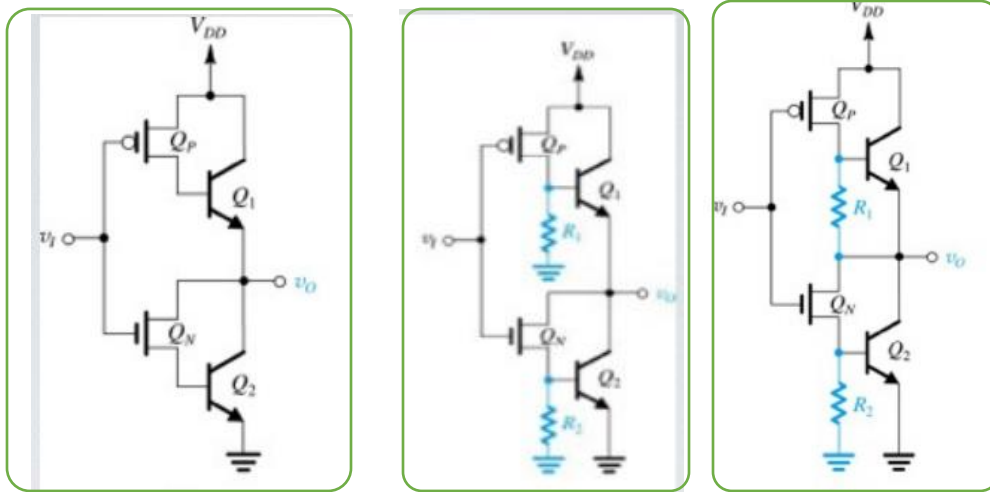


Fig. 3 (a)

(b)

(c)

- Using the figure of the BiCMOS circuit (fig c) with a capacitor load of 45 calculate t_{phl} (propagation from high to low)
- Calculate the output current of fig. (fig c) when $V_{out} = (V_{OH} + V_{OL})/2$

ANSWER SHEET:

1.
- a. Function: _____

b. V_{OH} = _____ V_{OL} = _____

c. $t_r, (t \text{ rise})$ = _____

2.
- Schematic

a. Graph

- b. $(W/L)_N$: _____ $(W/L)_P$: _____

c. V_{OH} : _____ V_{OL} : _____ t_{phl} (propagation from high to low): _____

3.
- a. V_R = _____

4.
- a. t_{phl} (propagation from high to low)= _____

b. I_{out} = _____